

APPENDIX 5 – DERIVATION OF EQUATIONS 6-1 AND 6-2

I derived these equations to determine the power transmitted through a transmission line with attenuation and terminated in a mismatch (see Fig Appendix 5-1).

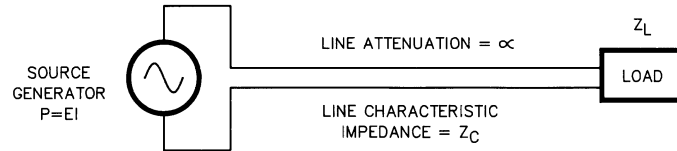


Fig Appendix 5-1 – Illustrating the transmission line for the Appendix 5 derivation of Eqs 6-1 and 6-2.

$$\begin{aligned} \rho_L &= \text{voltage reflection coefficient at load} \\ &= \frac{Z_L - Z_C}{Z_L + Z_C} = \frac{\text{SWR} - 1}{\text{SWR} + 1} \quad (\text{Eqs 3-1 and 3-2}) \end{aligned}$$

$$\rho_I \text{ at line input} = \rho \varepsilon^{-2\alpha}$$

$$\rho_I^2 \text{ at line input} = \rho^2 \varepsilon^{-4\alpha}$$

$$\rho_L^2 = \text{power reflection coefficient at load (equals reflected power)}$$

where

$$\alpha = \text{line attenuation in nepers} = \frac{\text{dB}}{20 \log \varepsilon} = \frac{\text{dB}}{8.6859}$$

(one neper = 0.115129 decibel)

$$\varepsilon = 2.718282$$

(the base of natural logarithms)

The forward *voltage* wave encounters a reduction in level by the loss factor of $1/\varepsilon^\alpha$, or $\varepsilon^{-\alpha}$ in traveling from the source to the load. The reflected voltage wave encounters the same reduction factor $\varepsilon^{-\alpha}$ in its return to the source. Hence, the voltage reflection coefficient at the line input is $\rho_I = \rho \varepsilon^{-2\alpha}$.

The forward *power* encounters a *one-way* attenuation-loss factor $\varepsilon^{-2\alpha}$. Power returning to the source from a load reflection encounters a *two-way* loss — once during the trip to the load, and again during its return to the source. The power reflection coefficient at the line input is therefore $\rho_I^2 = \rho^2 \varepsilon^{-4\alpha}$.

Let power supplied by the source = 1, and let reflected power reaching the input (which adds to the source power) = r. Then,

$$1 + r = \text{total forward power at line input,}$$

$(1 + r)\epsilon^{-2\alpha}$ = forward power arriving at the load, and

$$\frac{r}{1+r} = \text{input power reflection coefficient} = \rho^2 = \rho^2 \epsilon^{-4\alpha}.$$

Now let $\frac{r}{1+r}$ (and $\rho^2 \epsilon^{-4\alpha}$) = a.

$$\text{Then, total forward power } (1 + r) \text{ at the line input} = 1 + \frac{a}{1-a} = \frac{1-a+a}{1-a} = \frac{1}{1-a}.$$

Hence, it follows that

Forward power at line input	→	Forward power at load after line atten.	–	Power reflected at load	=	Power absorbed in load
$1 + r$	→	$(1 + r)\epsilon^{-2\alpha}$	–	$\rho^2(1 + r)\epsilon^{-2\alpha}$	=	$(1 + \rho^2)(1 + r)\epsilon^{-2\alpha}$

and

$$\frac{1}{1-a} \rightarrow \frac{\epsilon^{-2\alpha}}{1-a} - \frac{\rho^2 \epsilon^{-2\alpha}}{1-a} = \frac{(1-\rho^2)\epsilon^{-2\alpha}}{1-a}$$

But $a = \rho^2 \epsilon^{-4\alpha}$, so by substitution we have Eq 6-1:

$$\frac{1}{1-\rho^2 \epsilon^{-4\alpha}} \rightarrow \frac{\epsilon^{-2\alpha}}{1-\rho^2 \epsilon^{-4\alpha}} - \frac{\rho^2 \epsilon^{-2\alpha}}{1-\rho^2 \epsilon^{-4\alpha}} = \frac{(1-\rho^2)\epsilon^{-2\alpha}}{1-\rho^2 \epsilon^{-4\alpha}}.$$

Translating the last expression on the right, it means that power absorbed in the load equals the source power times the quantity

$$\frac{(1 - \rho^2) \text{ times one - way line - attenuation factor}}{1 - (\rho^2 \text{ time two - way line - attenuation factor})}$$

where $\rho = \rho_L$ from Eqs 3-1 and 3-2 above.

$$\frac{1}{1-\rho^2} \rightarrow \frac{1}{1-\rho^2} - \frac{\rho^2}{1-\rho^2} = 1$$

$$1 + r \rightarrow 1 + r - r = 1$$

When the SWR on a transmission line is $\approx 4.6:1$ the total attenuation α_T is approximately two-times the attenuation of the line when matched.

Appendix 5-2